



# **SRI SHANMUGHA COLLEGE OF ENGINEERING AND TECHNOLOGY**

**SANKARI, SALEM**

**DEPARTMENT OF BIOMEDICAL ENGINEERING**

**Academic year 2021-2022 Odd Semester**

**(Regulation 2017)**

**III SEMESTER - BME**

**BM8312- DEVICES AND CIRCUITS LABORATORY**

**LAB MANUAL**

**PREPARED BY**

**Mr. RANJITH KUMAR T**

**AP/ECE**

**LIST OF EXPERIMENTS**

1. Characteristics of PN Junction Diode
2. Zener diode Characteristics & Regulator using Zener diode
3. Common Emitter input-output Characteristics
4. Common Base input-output Characteristics
5. FET Characteristics
6. SCR Characteristics
7. Clipper and Clamper & FWR
8. Verifications of Thevenin & Norton theorem
9. Verifications of KVL & KCL
10. Verifications of Super Position Theorem
11. Verifications of Maximum power transfer & Reciprocity theorem
12. Determination of Resonance Frequency of Series & Parallel RLC Circuits
13. Transient analysis of RL and RC circuits

### **BEYOND THE SYLLABUS**

- Characteristics of UJT

#### **Ex.No.1**

### **CHARACTERISTICS OF PN JUNCTION DIODE**

#### **Aim:**

To determine the VI characteristics of PN Diode

#### **Apparatus required:**

S.No	Name	Range	Type	Qty
1	R.P.S	(0-30)V		1


2	Ammeter	(0-5)mA, (0-25)mA		1 1
3	Voltmeter	(0-10)V (0-1 )V		1 1
4	Connecting wires	-		As Required
5	Bread Board			1
6	Resistors	1K $\Omega$		1
7	Diode- PN	BY127		1

### **THEORY:**

A diode is a PN junction formed by a layer of P type and layer of N type Semiconductors. Once formed the free electrons in the N region diffuse across the junction and combine with holes in P region and so a depletion Layer is developed. The depletion layer consists of ions, which acts like a barrier for diffusion of charged beyond a certain limit. The difference of potential across the depletion layer is called the barrier potential. At 2.5degree the barrier potential approximately equal 0.7v for silicon diode and 0.3v for germanium diode.


When the junction is forward bias, the majority carrier acquired sufficient energy to overcome the barrier and the diode conducts. When the junction is reverse biased the depletion layer widens and the barrier potential increases. Hence the Majority carrier cannot cross the junction and the diode does not conduct. But there will be a leakage current due to minority carrier. When diode is forward biased, resistance offered is zero, and when reverse biased resistance offered is infinity. It acts as a perfect switch.

### **PIN DIAGRAM:**

 


### **CIRCUIT DIAGRAM:**

### **FORWARD BIAS:**

 

**REVERSE BIAS:**

 

**PROCEDURE:**

**FORWARD BIAS:**

1. The connections are made as per the circuit diagram.
2. The positive terminal of power supply is connected to anode of the diode and negative terminal to cathode of the diode.
3. Forward voltage  $V_f$  across the diode is increased in small steps and the forward current is noted.
4. The readings are tabulated. A graph is drawn between  $V_f$  and  $I_f$ .

**REVERSE BIAS :**

1. The connections are made as per the circuit diagram.

2. The positive terminal of power supply is connected to cathode of the diode and negative terminal to anode of the diode.
3. Reverse voltage  $V_r$  across the diode is increased in small steps and the Reverse current is noted.
4. The readings are tabulated. A graph is drawn between  $V_r$  and  $I_r$ .

**TABULATION:**


**FORWARD BIAS:**

$V_f(\text{volts})$	$I_f(\text{mA})$

**REVERSE BIAS:**

$V_r(\text{volts})$	$I_r(\text{mA})$

**MODEL GRAPH**

 

### **PRE REQUISITE:**

1. What is a semiconductor?
2. Write the Diode current Equation.
3. What is the value of  $V_t$  at room temperature
4. What is meant by forward bias
5. What is meant by reverse bias?

### **REVIEW QUESTIONS:**

1. How a PN junction is formed?
2. In what way the width of depletion region can be varied?
3. What is potential barrier?
4. In forward bias condition the current condition is due to \_\_\_\_\_
5. What is reverse saturation current  $I_{co}$ ?

### **RESULT:**

Thus the characteristics of PN-Junction diode were drawn.

**Ex.No.2a**

## **CHARACTERISTICS OF ZENER DIODE**

### **Aim:**

To determine the VI characteristics of Zener Diode

**APPARATUS REQUIRED:**


S.No	Name	Range	Type	Qty
1	R.P.S	(0-30)V		1
2	Ammeter	(0-30) mA		1
3	Voltmeter	(0-10)V (0-1 )V		1 1
4	Connecting wires	-		As Required
5	Bread Board			1
6	Resistors	1K $\Omega$		1
7	Diode- Zener	FZ 5V6/ FZ 6V2		1

**THEORY:**

Zener diodes have many of the same basic properties of ordinary semiconductor diodes. When forward biased, they conduct in the forward direction and have the same turn on voltage as ordinary diodes. For silicon this is about 0.6 volts.


In the reverse direction, the operation of a Zener diode is quite different to an ordinary diode. For low voltages the diodes do not conduct as would be expected. However, once a certain voltage is reached the diode "breaks down" and current flows. Looking at the curves for a Zener diode, it can be seen that the voltage is almost constant regardless of the current carried. This means that a Zener diode provides a stable and known reference voltage. Hence they are used as Voltage regulators.

**PIN DIAGRAM:**

 


**CIRCUIT DIAGRAM:**

**FORWARD BIAS:**

 

**REVERSE BIAS:**

 

**PROCEDURE:**

**FORWARD BIAS:**

1. The connections are made as per the circuit diagram.
2. The positive terminal of power supply is connected to anode of the diode and negative terminal to cathode of the diode.
3. Forward voltage  $V_f$  across the diode is increased in small steps and the forward current is noted.
4. The readings are tabulated. A graph is drawn between  $V_f$  and  $I_f$ .

**REVERSE BIAS:**

1. The connections are made as per the circuit diagram.
2. The positive terminal of power supply is connected to cathode of the diode and negative terminal to anode of the diode.
3. Reverse voltage  $V_r$  across the diode is increased in small steps and the Reverse current is noted.
4. The readings are tabulated. A graph is drawn between  $V_r$  and  $I_r$ .

**TABULAR COLUMN:**


**FORWARD BIAS:**

$V_f(\text{volts})$	$I_f(\text{mA})$

**REVERSE BIAS:**

$V_r(\text{volts})$	$I_r(\text{mA})$

**MODEL GRAPH**

 

**PRE REQUISITE:**

1. How the name of the Zener came?
2. What is cause of reverse breakdown?
3. What is Zener voltage?
4. Write the Symbol for the Zener diode.
5. What are the different types of breakdowns in semiconductor junctions?

**REVIEW QUESTIONS:**

1. What is the difference between p-n Junction diode and Zener diode
2. Can we use Zener diode as a switch?
3. Explain working of a Zener Diode
4. What is the max value of voltage of Zener breakdown devices
5. What is cause of reverse breakdown

**RESULT:**

Thus the characteristics of Zener diode were drawn.

**Ex.No.2b**

## ZENER DIODE AS A VOLTAGE REGULATOR

### Aim:

To study the Zener Diode as Voltage Regulator.

### APPARATUS REQUIRED:


S.No	Name	Range	Type	Qty
1	R.P.S	(0-30)V		1
2	Ammeter	(0-30) mA		1
3	Voltmeter	(0-10)V (0-1 )V		1 1
4	Connecting wires			As Required
5	Bread Board			1
6	Resistors	1K $\Omega$		1
7	Diode- Zener	FZ 5V6/ FZ 6V2		1

### THEORY:


Zener diodes have many of the same basic properties of ordinary semiconductor diodes. When forward biased, they conduct in the forward direction and have the same turn on voltage as ordinary diodes. For silicon this is about 0.6 volts.

In the reverse direction, the operation of a Zener diode is quite different to an ordinary diode. For low voltages the diodes do not conduct as would be expected. However, once a certain voltage is reached the diode "breaks down" and current flows. Looking at the curves for a Zener diode, it can be seen that the voltage is almost constant regardless of the current carried. This means that a Zener diode provides a stable and known reference voltage. Hence they are used as Voltage regulators.

### PIN DIAGRAM:

 

### CIRCUIT DIAGRAM:

 

**PROCEDURE:**

1. The connections are made as per the circuit diagram.
2. Keep Load resistance  $R_L$  constant.
3. Vary the Input voltage and note down the corresponding output voltage.
4. Now keep voltage constant vary the  $R_L$  and note down the voltmeter corresponding reading.
5. Plot the respective regulations graph.

**TABULAR COLUMN:**


**LOAD REGULATION:**

$R_L$ (k $\Omega$ )	Vout (V)


**LINE REGULATION:**

$V_{in}$ (V)	$V_{out}$ (V)

**MODEL GRAPH**

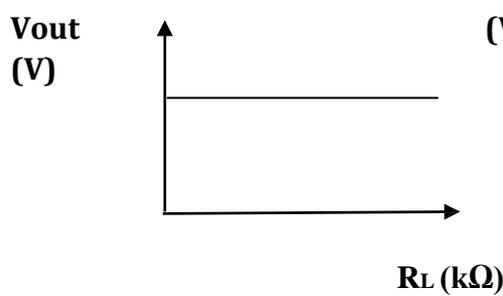

**LOAD REGULATION**

 

**LINE REGULATION**

**PREREQUISITE**

1. How Zener diode acts as a voltage regulator.
2. Explain working of a Zener Diode
3. Compare Zener and avalanche Breakdown.

**REVIEW QUESTIONS:**

1. What are the applications of Zener diode?
2. What is voltage regulator?
3. What is cut-in-voltage?
4. What is break down voltage?
5. Draw characteristics of Zener Diode under Forward & Reverse Bias Conditions

**RESULT:**

Thus the Zener diode as a Voltage Regulator were studied.

**Ex.No:3****CHARACTERISTICS OF CE CONFIGURATION****AIM:**


To plot the transistor characteristics (INPUT & OUTPUT) of CE configuration.


**APPARATUS REQUIRED:**

S.No.	COMPONENTS	SPECIFICATION	QTY
1	Transistor BC 107	Max Rating : 50V 1A, 3W	1
2	Resistors	10K $\Omega$ ,100 $\Omega$	2
3	Regulated power supply	(0-30) V	1
4	Voltmeters	Mc (0-10) V Mc (0-1) V	1 1
5	Ammeters	Mc (0-30) mA Mc (0-100) $\mu$ A	1 1
6	Bread board & connecting wires		As Required

**THEORY:**

A NPN function transistor consist of a silicon (or germanium) crystal in which a layer of p – type silicon is sandwiched between two layers of N – type silicon. The arrow on emitter lead specifies the direction of the current flow when the emitter – base functionis biased in the forward direction since the conductivity of the BJT depends on both the majority and minority carriers it is called bipolar device. In CE configuration, Emitter is common to both the Emitter and Base.

  **PIN DIAGRAM OF BC107****CIRCUIT DIAGRAM:**



**DESCRIPTION:**

**Input Characteristics:**

Voltage across Base Emitter junction  $V_{BE}$  vs  $I_B$ , where  $V_{CE}$  constant

**Output Characteristics:**

Voltage across Collector Emitter junction  $V_{CE}$  vs  $I_C$  where  $I_B$  constant

**PROCEDURE:**

**Input Characteristics:**

1. Connections are made as per the circuit diagram.
2.  $V_{CE}$  is kept constant (say 2V),  $V_{BE}$  is varied in steps of 0.1V and the corresponding  $I_B$  values are tabulated. The above procedure is repeated for 1V etc.
3. Graph is plotted between  $V_{BE}$  vs  $I_B$ , where  $V_{CE}$  constant.

**Output Characteristics:**

1. Connection are made as per the circuit diagram
2.  $I_B$  is kept constant,  $V_{CE}$  is varied in step IV the corresponding  $I_C$  values are tabulated. The above procedure is repeated for different constant values.
3. Graph is plotted between  $V_{CE}$  and  $I_C$  for a constant  $I_B$ .

**TABULATION:**


**Input Characteristics:**

$V_{CE} = V$		$V_{CE} = V$	
$V_{BE}(V)$	$I_B (\mu A)$	$V_{BE}(V)$	$I_B (\mu A)$

**Output characteristics:**

$I_B = \mu A$		$I_B = \mu A$	
$V_{CE}(V)$	$I_C (mA)$	$V_{CE}(V)$	$I_C (mA)$

**MODEL GRAPH:**

 

**PRE REQUISITE:**

1. List the current components of BJT in CE configuration
2. What is Early Effect?
3. Why the doping of collector is less compared to emitter?
4. What do you mean by “reverse active”?
5. What is the difference between CE and Emitter follower circuit?

**REVIEW QUESTIONS:**

1. Explain the operation of CE configuration
2. Determine the output resistance and input resistance
3. Define current gain in CE configuration?
4. Why CE configuration is preferred for amplification

## **RESULT:**

Thus the input and output characteristic of BJT in Common Emitter mode is drawn.

## **Ex.No:4**

### **CHARACTERISTICS OF CB CONFIGURATION**

## **AIM:**

To plot the transistor characteristics (INPUT & OUTPUT) of CB configuration.

## **APPARATUS REQUIRED:**

S.No.	COMPONENTS	SPECIFICATION	QTY
1	Transistor BC 107	Max Rating : 50V 1A, 3W	1
2	Resistors	470 $\Omega$	2
3	Regulated power supply	(0-30) V	1
4	Voltmeters	Mc (0-10) V Mc (0-1) V	1 1
5	Ammeters	Mc (0-30) m A	2
6	Bread board & connecting wires	-	1


## **THEORY:**

A NPN function transistor consist of a silicon (or germanium) crystal in which a layer of p – type silicon is sandwiched between two layers of N – type silicon. The arrow on emitter lead specifies the direction of the current flow when the emitter – base functionis biased in the forward direction since the conductivity of the BJT depends on both the majority and minority carriers it is called bipolar device. In CB configuration, base is common to both the emitter and collector.

## **PIN DIAGRAM OF BC107**



## **CIRCUIT DIAGRAM:**

 

**DESCRIPTION:**

**Input Characteristics:**

Voltage across Base Emitter junction  $V_{BE}$  vs  $I_E$ , where  $V_{CB}$  constant

**Output characteristics:**

Voltage across Collector Emitter junction  $V_{BC}$  vs  $I_C$  where  $I_E$  constant

**PROCEDURE:**

**Input Characteristics:**

1. Connections are made as per the circuit diagram.
2.  $V_{CB}$  is kept constant (say 2v),  $V_{BE}$  is varied insteps of 0.1v and the corresponding  $I_E$  values are tabulated. The above procedure is repeated for 1V etc.
3. Graph is plotted between  $V_{BE}$  vs  $I_E$ , where  $V_{CB}$  constant.

**Output Characteristics:**

1. Connection are made as per the circuit diagram
2.  $I_E$  is kept constant,  $V_{BC}$  is varied in step IV the corresponding  $I_C$  values are tabulated. The above procedure is repeated for different constant values.
3. Graph is plotted between  $V_{BC}$  and  $I_C$  for a constant  $I_E$ .

**TABULATION:**

**Input Characteristics:**


$V_{CB} = V$		$V_{CB} = V$	
$V_{BE}$ (V)	$I_E$ (mA)	$V_{BE}$ (V)	$I_E$ (mA)

--	--	--	--

**Output Characteristics:**

$I_E = \text{mA}$		$I_E = \text{mA}$	
$V_{BE} \text{ (V)}$	$I_C \text{ (mA)}$	$V_{BE} \text{ (V)}$	$I_C \text{ (mA)}$

**MODEL GRAPH:**

 

**PRE REQUISITE:**

1. Explain the operation of CB configuration
2. Determine the output resistance
3. Determine input resistance
4. Explain input characteristics
5. Explain output characteristics

**REVIEW QUESTIONS:**

1. Bring out the comparison of CC and CB transistor parameters
2. Give the relation of Ebers moll equation.
3. Bring out the comparison of CE and CB transistor parameters

4. Draw input and output characteristics of CB?
5. Explain Gummel poll model

**RESULT:**

Thus the input and output characteristic of BJT in Common Base mode is drawn.

**EX .NO-5**

**CHARACTERISTICS OF JFET.**

**AIM:**

To plot the drain and transfer characteristics of JFET & to find drain resistance, trans conductance, amplification factor, drain saturation current  $I_{DSS}$  and Pinch off voltage.

**APPARATUS REQUIRED:**


S.No.	Components	Specification	Qty
1	FET	BFW10 $I_{dss} > 8 \text{ mA}$ , $V_p < 8V$	1
2	Resistors	$1K\Omega$	1
3	Regulated dual power supply	MC (0-30)V	1
4	Voltmeters	MC (0-10)V MC (0-25)V	1 1
5	Ammeters	MC (0-25) mA	1
6	Bread board & connecting wires		

**THEORY:**


Field effect transistor is a semiconductor device that depends for its operation on the control of current by an electric field. It's operation depends on the flow of majority carriers only. It is therefore a unipolar device. It exhibits a high input resistance. An N- channel JFET

consists of a N-type bar is sandwiched between two heavily doped Persians. Due to the concentration gradient, the depletion region formed. On both sides of the semiconductor bar the ohmic contacts are made. One terminal is called source & other is called drain. Both the p-type regions are connected together.

### PIN DIAGRAM OF BFW10

 

### CIRCUIT DIAGRAM

 

### DESCRIPTION:

### DRAIN CHARACTERISTICS

INPUT: Drain voltage  $V_{DS}$  is varied in steps of 1V,  $V_{GS}$  is kept constant OUTPUT:

Drain current  $I_D$

### TRANSFER CHARACTERISTICS

INPUT: Gate – source voltage  $V_{GS}$  is varied, Drain –source voltage  $V_{DS}$  is kept constant OUTPUT:

Drain current  $I_D$

**PROCEDURE:**

**Drain Characteristics:**

1. Connections are made as per the circuit diagram.
2. Gate –source voltage  $V_{GS}$  is kept constant (say  $-1v$ ), drain voltage  $V_{DS}$  is varied in steps of  $1v$  and the corresponding drain current  $I_D$  values are tabulated.
3. The above procedure is repeated for  $V_{GS} = -2v, 0v$ .
4. The graph is plotted  $V_{DS}$  and  $I_D$  for a constant  $V_{GS}$ . 5. The drain resistance is found from the graph

$$r_d = \Delta V_{DS} / \Delta I_D$$

**Transfer Characteristics:**

1. Connections are made as per the circuit diagram.
2. Drain –source voltage  $V_{DS}$  is kept constant (say  $5v$ ), the gate – source voltage  $V_{GS}$  is varied in steps of  $1v$  (-VE voltage) and the corresponding drain current  $I_D$  values are tabulated.
3. The above procedure is repeated for  $V_{DS} = 10v, 15v$ , 4. Graph is plotted between  $V_{GS}$  and  $I_D$  for a constant  $V_{DS}$ .
5. The trans conductance is found from the graph

$$g_m = \Delta I_D / \Delta V_G$$

**TABULAR COLUMN:**

**Drain characteristics**


$V_{GS} = V$		$V_{GS} = V$	
$V_{DS} (V)$	$I_D (mA)$	$V_{DS} (v)$	$I_D (mA)$

**Transfer characteristics**

$V_{DS} = V$		$V_{DS} = V$	
$V_{GS} (V)$	$I_D (mA)$	$V_{GS} (V)$	$I_D (mA)$


## MODEL GRAPH:

### DRAIN CHARACTERISTICS

 

$V_{DS}$  (v)

### TRANSFER CHARACTERISTICS

 

$I_D$   
(mA)

$V_{GS}$  (v)

## CALCULATION

Transconductance  $g_m = \Delta I_D / \Delta V_G$

Drain resistance  $r_d = \Delta V_{DS} / \Delta I_D$  Amplification factor

$\mu = g_m r_d$

## PRE REQUISITE:

1. Why it is called by name “field effect transistor”?
2. What are the advantage of FET OVER BJT?
3. What are the disadvantages of FET?
4. What is the significance of arrowhead in FET symbol?
5. Why FET is called unipolar device

## REVIEW QUESTIONS:

1. Define VVR.
2. Why MOSFET is preferred than FET?
3. What are the differences between FET & MOSFET?
4. What are the applications of FET?
5. Why FET is called us voltage controlled device?

## **RESULT:**

Thus the drain and transfer for characteristics of JFET is drawn.

Drain resistance  $r_d =$

Trans conductance  $g_m =$

Amplification factor =

## **EX NO: 6**

### **CHARACTERISTICS OF SCR**

## **AIM:**

To construct a circuit using SCR to draw its Firing Characteristics.

## **APPARATUS REQUIRED:**

<b>S.No</b>	<b>Components</b>	<b>Specification</b>	<b>Quantity</b>
1	SCR	TYN410	1
2	Dual RPS	(0-30)V	1
3	Resistor	560 $\Omega$ , 470 $\Omega$ (0.5W)	1 each
4	Ammeter	(0-25)mA (0-100)mA	1 1
5	Voltmeter	(0-30)V	1
6	Bread board		1

## **THEORY:**

The SCR consists of four layers of semiconductor material alternatively P type and N type. It can be brought of as an ordinary rectifier with a control element .The control element is called GATE. The gate current determines the anode to cathode voltage at which the device starts to conduct.


It means that gate terminal of the SCR is controlled by the applied voltage. Once switched ON the gate has no further control. To switch the SCR the anode current has to be reduced below a certain level called HOLDING CURRENT.

The SCR can be triggered ON with the gate or amplitude triggering, pulse triggering methods. The terms ON & OFF are used to represent the conduction and blocking mode of


SCR respectively open circuited with the anode to cathode voltage made large enough .In conduction state the SCR behaves as an ordinary diode.

The anode to cathode voltage at which the SCR conducts is called BREAK OVER VOLTAGE or FORWARD BLOCKING VOLTAGE. It has great switching speed than other devices.

### PIN DIAGRAM:

 

### CIRCUIT DIAGRAM:

 


### PROCEDURE:

1. Give the circuit connections as per the diagram.
2. Set  $V_{AK}$  to 10V using RPS<sub>1</sub>
3. Increase Gate Current using RPS<sub>2</sub> till the  $V_{AK}$  suddenly drops down. Note the gate current at this point. This is known as firing current.
4. Set the firing current in  $I_G$ .
5. Increase the Anode voltage using RPS<sub>1</sub> in steps so that both  $I_A$  increases. Note down change in  $V_{AK}$ .
6. Note the maximum  $I_A$ . This is known as Holding current ( $I_H$ ).
7. Remove the Gate terminal (ie). Make the gate open.
8. Anode current drops now and reaches minimum which is called Latching current ( $I_L$ ).

**TABULAR COLUMN:**

	$V_{AK} = v$	$I_A$ (mA)	$I_G$ (mA)
Before Firing			
At Firing			
After Firing			

**MODEL GRAPH:**

 

**PRE REQUISITE:**

1. What is an SCR?
2. What are the methods to trigger ON SCR?
3. What is meant by break over voltage of SCR?
4. What is meant by holding current and latching current in SCR?
5. SCR a unidirectional or bidirectional device.

**REVIEW QUESTIONS:**

1. What is meant by Valley Point and Peak point
2. After triggering an SCR, the gate pulse is removed. What is the state (ON or OFF) of the device at this condition? Justify our answer
3. Why is Peak Reverse Voltage Important?

4. What is asymmetrical SCR?
5. What is the difference between SCR and TRIAC?

**RESULT:**

Thus the characteristics of the SCR is drawn.

Forward break over voltage =  
 Latching Current =  
 Holding Current =

**Ex.No:7**

**CLIPPER AND CLAMPER**

**AIM:**

To construct and study the operation of clipper and clamper circuits.

**APPARATUS REQUIRED:**

S.No	COMPONENTS	RANGE/SPECIFICATION	QUANTITY
1.	Resistor	4.7KΩ,100KΩ	1each
2.	Capacitor	0.1μf	1
3.	Diode	IN4001	1
4.	AFG	1MHz	1
5.	CRO	30MHz	1
6.	Bread Board		1
7.	Regulated power supply	(0 – 30 )V	1

**THEORY:**


The basic action of a clipper circuit is to remove certain portions of the waveform, above or below certain levels as per the requirements. Thus the circuits which are used to clip off unwanted portion of the waveform, without distorting the remaining part of the waveform are called clipper circuits or Clippers. The half wave rectifier is the best and simplest type of clipper circuit which clips off the positive/negative portion of the input signal. The clipper circuits are also called limiters or slicers.

**PROCEDURE**


## Clipper Circuit

1. Connect the components and apparatus as shown in the circuit diagram.
2. Set input, sinusoidal signal of 8Vp-p and 1 kHz frequency and the reference voltage as 2V using RPS.
3. Observe the output across the diode using CRO.
4. Plot the input and output signal in a linear graph.

### NEGATIVE PEAK CLIPPER

 

### MODEL GRAPH

 

### Theoretical calculations:

$$V_r=2v, V_\gamma=0.6v$$

When the diode is forward biased  $V_o = -(V_r + V_\gamma) = -(2v + 0.6v) = -2.6v$

When the diode is reverse biased the  $V_o = V_i$


### **PROCEDURE**


#### **Clamper Circuit**

1. Connect the components and apparatus as shown in the circuit diagram.
2. Set input, sinusoidal signal of 8Vp-p and 1kHz frequency
3. Observe the output across the load resistance using CRO.
4. Plot the input and output signal in a linear graph.

### **CIRCUIT DIAGRAM**


#### **POSITIVE CLAMPER**

 


 

**CIRCUIT DIAGRAM**

**NEGATIVE CLAMPER**

 

 

### **PRE REQUISITE**

1. What is clipper?
2. What is clamper?
3. Difference between clipper and clamper?
4. What are different types of clampers?
5. Positive base and negative base clippers means

### **REVIEW QUESTIONS:**

1. How does a clamper circuit add a dc level to the output voltage?
2. What do you mean by biased and combinational clipper?
3. What are the classifications of a clipper circuit?
4. Why capacitors are used in clampers?
5. What happens in the output waveform if the polarity of capacitor is changed in the clampers

## **RESULT:**

Thus the clipper and clamper circuits are designed and the output waveforms are observed.

## **Ex.No:8**

## **VERIFICATION OF THEVENIN'S & NORTON'S THEOREM**

### **AIM:**

- To verify the Thevenin's theorem for the given electric circuit.
- To verify the Norton's theorem for the given circuit.

## **THEVENIN'S THEOREM**

### **STATEMENT:**

A one port linear, active, resistive network which contains one or more voltage or current sources can be replaced by a single voltage source  $V_{th}$  in series with a single resistance  $R_{th}$ .  $V_{th}$  is equal to the open circuit voltage across the port terminals of the network & the resistance  $R_{th}$  is measured between the port terminals with all the energy sources replaced by their internal resistance.



$R_{th}$  - Thevenin's resistance.  $V_{th}$  - Thevenin's voltage.


### **APPARATUS REQUIRED:**

S.No	Name	Range	Qty
1	R.P.S	(0-30) V	1
2	Ammeter	0-50 mA	2
3	Voltmeter	0 – 25V	2
4	Connecting wires		
5	Resistors	1K, 2.2K, 3.3K, 4.7K, 6.8K, 10K	Each 2
6	Breadboard		1


### **PROCEDURE:**

1. To Find  $V_{th}$  :( Under open circuit the load resistance)
  - a) Connections are made as per the circuit diagram.
  - b) Switch on the power supply and note down the voltmeter readings  $V_{th}$ .
  
2. To Find  $R_{th}$  (Under short circuit Voltage source)
  - a) Connections are given as per the circuit diagram.
  - b) Switch ON the Power supply.
  - c) Vary the R.P.S to fixed voltage, note down the ammeter and voltmeter readings.
  - d) Repeat the step (ii) for various R.P.S voltage and tabulate the readings.
  
3. To Find  $I_L$ 
  - a) Connections are given as per the circuit diagram.
  - b) Switch ON the power supply.
  - c) Vary the R.P.S. to the given voltage and note down the ammeter reading ( $I_L$ ).


### **CIRCUIT DIAGRAM: I**

 

To find  $R_{th}$ :

 

**Thevinin's Equivalent Circuit:**

 


$$I_L = \frac{V_{th} R_L}{R_{TH} + R_L}$$


**TABULATION:**

S.No	Specified voltage (Volts)	Theoretical			Practical		
		Vth	Rth	IL	Vth	Rth	IL

**CIRCUIT DIAGRAM: II**

 


**CIRCUIT DIAGRAM: III**

 

**B. NORTON'S THEOREM**

 **Statement:**

A one port linear, active, resistive network which contains one or more voltage or current sources can be replaced by a single current source  $I_{sc}$  in parallel with a single resistance  $R_{th}$ .  $I_{sc}$  is equal to the short circuit current across the port terminals of the network & the resistance  $R_{th}$  is measured between the port terminals with all the energy sources replaced by their internal resistance.



Where,

$I_{sc}$  – Short circuit current at terminals A & B  
 $R_{th}$  – Thevenin's equivalent Resistance.


### Apparatus Required:

S.No	Name	Range	Qty
1	R.P.S	(0-30) V	1
2	Ammeter	0 – 50mA	2
3	Voltmeter	0-25 V	2
4	Connecting wires		
5	Resistors	1K, 2.2K,4.7K,6.8K	Each 2
6	Breadboard		1

### Procedure:


- To find  $I_{SC}$ (short circuit the load resistance)
  - Connections are made as per the circuit diagram.
  - Note down the ammeter reading ( $I_{SC}$ )
- To find  $R_{th}$ (short circuit the voltage source)
  - Connections are made as per the circuit diagrams
  - Supply is switched 'ON'
  - Vary the R.P.S to the specified voltage, note down the ammeter and voltmeter readings.
  - Repeat the step 3 for various R.P.S voltage and the readings are tabulated.
  - Calculate the  $R_{Th}$  using the tabulation.
- To Find  $I_L$ 
  - Connections are given as per the circuit diagram.
  - Switch ON the power supply.
  - Vary the R.P.S. to the specified voltage and note down the ammeter reading ( $I_L$ ).

### Circuit diagram:

 

### Theoretical Verification:

**To Find I<sub>sc</sub>:**

 


35

$$\begin{array}{l}
 \square 1 \\
 \square 2
 \end{array}
 \left| \begin{array}{l}
 R_1 + R_2 \\
 R_1 + R_2
 \end{array} \right.
 \left. \begin{array}{l}
 - R_2 \\
 - R_2
 \end{array} \right|
 \begin{array}{l}
 R_2 + R_3 \\
 0
 \end{array}$$


$$I_{sc} = I_2 = \square 2 / \square \square$$

**To Find R<sub>TH</sub>:**

 




**CIRCUIT DIAGRAM: II**

 

**CIRCUIT DIAGRAM: III**

 

### **PRE REQUISITE**

1. How  $R_{th}$  is obtained in any circuit for applying Thevenin's and Norton's theorem?
2. What is  $V_{th}$  or Thevenin's voltage?
3. How  $V_{th}$  is obtained in any circuit for applying Thevenin's theorem?
4. What is  $I_N$  or Norton's current?
5. How  $I_N$  is obtained?

### **Review Questions:**

1. State Thevenin's & Norton's theorem.
2. Draw the Thevenin's & Norton's equivalent circuit for 3. What is duality theorem?
4. Explain dependent sources and sources transformation.
5. Explain Star-Delta conversion

### **RESULT:**

Thus the Thevenin's & Norton's theorems are verified.

### **Ex.No.9**

## VERIFICATION OF KIRCHOFFS CURRENT LAW AND KIRCHOFF'S VOLTAGE LAW.

### Aim:

- (a) To verify the Kirchoff's current law.
- (b) To verify the Kirchoff's voltage law.

### Statement:

#### Kirchhoff's Current Law:

The algebraic sum of all the currents at any junction in an electric circuit is zero. In other words, the sum of the current flowing towards a junction is equal to the sum of the currents flowing away from it.

#### Kirchhoff's Voltage Law:

In any closed circuit, the algebraic sum of all the electromotive forces and the potential drops is equal to zero. In other words, for any closed path in a network, the algebraic sum of voltages is zero.

(i.e) sum of voltage drops = sum of voltage rises.

### Apparatus Required:


S.No	Name	Specification	Qty
1	R.P.S	(0-30V)	
2	Ammeter	0 – 50mA	1
3	Voltmeter	0 – 25V	1
4	Connecting wires		
5	Bread Board		
6	Resistors	100Ω, 560Ω, 470Ω, 2.2K,3.3K,4.7K	Each 2

### PROCEDURE (Both KCL & KVL)

1. Connections are made as per the circuit diagram.
2. Switch on the power supply.

3. Vary the R.P.S to a specified voltage and note down the corresponding ammeter and voltmeter readings.
4. Repeat the step 3 for various R.P.S voltage and tabulate the readings.
5. Switch off the power supply and remove the connections.

**Model circuit of KVL:**

 


$$V = IR_1 + IR_2$$

$$V = V_1 + V_2$$

**TABULATION:**

S.No	Vs(Volts)	V1(Volts)	v2(Volts)	Vt=V1+V2(Volts)

**Model Circuit of KCL:**

 

$$V = I_1R_1 = I_2R_2$$

At the Junction A:


$$I = I_1 + I_2$$

**TABULATION:**

S.No	Vs(volts)	I(A)	I <sub>1</sub> (A)	I <sub>2</sub> (A)	I=I <sub>1</sub> +I <sub>2</sub> (A)

**Practical circuit Diagrams:**

 1. For the circuit shown in figure, compute the value of currents I<sub>1</sub>, I<sub>2</sub>, I<sub>3</sub>, I<sub>4</sub>, and I<sub>5</sub> by using KVL and KCL. Verify the results experimentally.



**TABULATION:**

**KVL:**

S.No	Vs(Volts)	V1(Volts)	V2(Volts)	V3(Volts)	V4(Volts)	V5(Volts)

**Loop1:  $15 = V_1 + V_2$**

**Loop2:  $V_2 = V_3 + V_4$**

**Loop3:  $V_3 = V_5$**


**KCL:**

S.No	Vs(Volts)	I <sub>1</sub> (A)	I <sub>2</sub> (A)	I <sub>3</sub> (A)	I <sub>4</sub> (A)	I <sub>5</sub> (A)

**$I_1 = I_2 + I_3$**

**$I_3 = I_4 + I_5$**

 2. For the circuit given, find the values of currents I<sub>1</sub>, I<sub>2</sub>, and I<sub>3</sub> using KVL and KCL.



**TABULATION:**

**KVL:**

S.No	Vs(Volts)	V1(Volts)	v2(Volts)	v3(Volts)	v4(Volts)	v5(Volts)


LOOP1:  $20 = V_1 + V_2$ ; LOOP2:  $V_2 = V_3 + V_4 + 15$ ; LOOP3:  $15 + V_4 = V_5$

**KCL:**

S.No	Vs(Volts)	I <sub>1</sub> (A)	I <sub>2</sub> (A)	I <sub>3</sub> (A)	I <sub>4</sub> (A)	I <sub>5</sub> (A)

$I_1 = I_2 + I_3$ ;  $I_3 = I_4 + I_5$

 3. For the circuit shown in the figure determine the values of currents  $I_1$ ,  $I_2$  and  $I_3$  using KVL and KCL



**TABULATION:**

S.No	Vs(Volts)	V1(Volts)	v2(Volts)	v3(Volts)	v4(Volts)	v5(Volts)

--	--	--	--	--	--	--

**KVL:**

Loop1:  $10 = V_1 + V_2$ ; Loop2:  $V_2 = V_3 + V_4 - 15$ ; Loop3:  $V_5 = V_1 + V_3$

S.No	Vs	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>	I <sub>4</sub>	I <sub>5</sub>

**Preparatory Questions**

1. State KCL and KVL.
2. What is meant by short circuit and open circuit?
3. Two resistances with the value of R<sub>1</sub>, R<sub>2</sub> are connected in i) series and ii) parallel. What is the equivalent resistance?
4. Two inductors with the value of L<sub>1</sub>, L<sub>2</sub> are connected in i) series and ii) parallel. What is the equivalent inductance?
5. Two capacitors with the value of C<sub>1</sub>, C<sub>2</sub> are connected in i) series and ii) parallel. What is the equivalent capacitance?

**REVIEW QUESTIONS:**

1. Define Resistance, Inductance and capacitance.
2. Color coding of resistor.
3. Define active and passive elements
4. Define Unilateral and Bilateral elements.
5. Define linear and Non-Linear elements.

### **RESULT:**

Thus the Kirchoff's current law and Kirchoff's voltage law are verified.

**Ex.No:10**

### **VERIFICATION OF SUPERPOSITION THEOREM**

#### **Aim:**

To verify the superposition theorem for the given electric circuit.

#### **Statement:**

In a linear lumped element, bilateral electric circuit energized by two or more sources, the current in any resistor is equal to the algebraic sum of the separate currents in each resistor when each source act, separately.

The Voltage sources are short-circuited and the current sources are open circuited in order to replace the other sources by their respective internal resistances.

#### **Apparatus Required:**

S.No	Name	Range	Qty
1	R.P.S	(0-30) V	1
2	Ammeter	0 -50 mA	1
3	Voltmeter	0 – 25 V	1
4	Connecting wires		
5	Resistors	10K, 22K,5.8K	Each 2
6	Breadboard		1


#### **Procedure:**

**To Find I, I<sub>1</sub>& I<sub>2</sub>:**


1. Connections are given as per the circuit diagram.
2. Switch on the power supply.

3. Vary the RPS to the given voltage and note down the ammeter readings for fig (1), fig (2) & fig (3).

 
(a) When both  $V_{S1}$  &  $V_{S2}$  are active



(b) When  $V_{S1}$  acts alone

 

(c) When  $V_{S2}$  acts alone

 


**TABULAR COLUMN:**

$V_{S1}$ (volts)	$V_{S2}$ (volts)	Theoretical				Practical			
		I (mA)	$I_1$ (mA)	$I_2$ (mA)	$I = I_1 + I_2$ (mA)	I (mA)	$I_1$ (mA)	$I_2$ (mA)	$I = I_1 + I_2$ (mA)

 
### PRACTICAL CIRCUIT II:

Find the current in the  $2.2\text{ k}\Omega$  resistor between A & B for the network using superposition theorem. Verify the results experimental


 
### PRACTICAL CIRCUIT III:

Find the current in the  $4.7\text{ k}\Omega$  resistor between A and B for the network using superposition theorem.



### PREREQUISITE

1. Define Lumped and distributed elements
2. Define ohm's law
3. What is the equivalent resistance for the resistor if it is connected in series and parallel
4. What is the equivalent Capacitance for the capacitor if it is connected in series and Parallel
5. What is the equivalent Inductance for the Inductor if it is connected in series and parallel

### Review Questions:

1. State superposition theorem.
2. What is duality theorem?
3. Explain dependent sources and sources transformation.
4. Explain Star-Delta conversion
5. State voltage division rule & State current division rule.

**Result:**

Thus the superposition theorem is verified.

**Ex.No:11**

**VERIFICATION OF MAXIMUM POWER TRANSFER AND  
RECIPROCITY THEOREM**

**Aim:**

- a. To practically verify the maximum power transfer theorem for the network with the theoretical value.
- b. To practically verify the reciprocity theorem for the network with the theoretical calculation.

**THEORY:**

**Maximum power transfer theorem:**

This theorem states that maximum power will be delivered from a voltage source to a load when the load resistance is equal to the internal resistance of the source.

$$\text{Max. Power transferred} = \frac{V_{th}^2}{4 R_{th}}$$

**Apparatus Required:**


S.No	Name	Range	Qty
1	R.P.S	(0-30) V	1
2	Ammeter	0 – 50 mA	
3	Voltmeter	0 – 25V	
4	Connecting wires		
5	Resistors	1K, 2.2K,4.7K,6.8K	Each 2

**a. MAXIMUM POWER TRANSFER THEOREM:**

**PROCEDURE:**

1. Remove the portion of network through which power has to be transferred.
2. Name those terminals as A and B.
3. Calculate  $R_{th}$  by substituting all sources with internal resistance working back at network
4. Give the connections as per the circuit diagram.
5. By varying the DRB ( $R_L$ ) for values of  $R_L$ , measure the current through  $R_L$ .
6. Calculate the power delivered to  $R_L$ .
7. Verify resistance ( $R_L$ ) at  $P_{L(max)}$  is equal to  $R_{th}$ .

**CIRCUIT DIAGRAM:**

 


**TABULATION**

**Experimental values:**


$R_L \Omega$	$V_{th}(v)$	$P_{th} (w)$

**Model Graph:**

 

 
### Practical circuit II:

Determine the value of  $R_L$  using maximum power transfer theorem and also find the power transferred to the load. Verify the result experimentally.


 
### Practical circuit III:

Determine the value of  $R_L$  using maximum power transfer theorem and also find the power transferred to the load.



### Reciprocity Theorem:

In any linear bilateral network the ratio of voltage to current response, in any element to the input is constant even when the position of the input and output are interchanged.


### Apparatus Required:

S.No	Name	Range	Qty
1	R.P.S	(0-30) V	1
2	Ammeter	0 – 50 mA	1
3	Voltmeter	0 – 25V	1
4	Connecting wires		
5	Resistors	1K, 2.2K, 4.7K, 6.8K	Each 2
6	Breadboard		1


### Procedure:

1. Connections are given as per the circuit diagram.
2. Note down the ammeter reading and find the ratio of the output current and input voltage.
3. Interchange the position of ammeter and the voltage source.
4. Note down the ammeter reading and find the ratio of the output and input voltage.
5. Compare this value with the value obtained in step 2.

**CIRCUIT DIAGRAM: ORIGINAL NETWORKS**

 

 **Circuit 1: To Measure the Load Current**



$$R_{eq} = (R_3 + R_4) * R_2$$

$$+ R_1$$

$$(R_3 + R_4) + R_2$$

$$I_T = V / R_{eq}$$

$$I = I_T * R_2$$

$$((R_3 + R_4) + R_2)$$


**TABULATION**

**Experimental values: Theoretical values:**

V (Volts)	I (mA)	Z = V/I
0		
2		
4		
6		

V (Volts)	I (mA)	Z = V/I
0		
2		
4		
6		

 **Circuit 2: After Interchanging Positions of V and I**



$$R_{eq} = \frac{R_1 * R_2}{R_1 + R_2} + R_3 + R_4$$

$$I_T = V / R_{eq}$$

$$I = \frac{I_T * R_2}{R_1 + R_2}$$

**TABULATION**


**Experimental values: Theoretical Values**

V (Volts)	I (mA)	Z = V/I
0		
2		
4		
6		

V (Volts)	I (mA)	Z = V/I
0		
2		
4		
6		

 **PRACTICAL CIRCUIT II:**

Obtain current flowing through the 1.2 k Ω in the circuit and verify the reciprocity theorem.



### **PRE REQUISITE**

1. Define duality
2. What is transient state?
3. What is transient time?
4. What is natural response?
5. What is transient response?

### **Review Questions:**

1. State Maximum Power transfer theorem.
2. State reciprocity theorem?
3. What is duality theorem?
4. Explain dependent sources and sources transformation.
5. Explain Star-Delta conversion

## **RESULT:**

Hence the maximum power transfer and reciprocity theorem for the given networks are practically verified.

## **Ex.No:12**

### **FREQUENCY RESPONSE OF SERIES AND PARALLEL RESONANCE CIRCUITS**

## **Aim:**

To plot the current vs frequency graph of series and parallel resonance circuits and hence measure the bandwidth, resonant frequency.

## **Apparatus Required:**

Sl. No	Name	Range	Qty
1.	Signal Generator	2MHz	1
2.	CRO	30MHz	1
3.	Connecting Wires		
4.	Resistors	1K, 470Ω, 100Ω	1 each
5.	Capacitors	0.01uF, 0.1μf	2
6.	Inductors	99mH, 300mH	1
7.	Bread Board		1

## **Circuit Description For RLC Series Circuit:**

A circuit is said to be in resonance when applied voltage V and current I are in phase with each other. Thus at resonance condition, the equivalent complex impedance of the circuit consists of only resistance (R). So current is maximum. Since V and I are in phase, the power factor is unity.

When the frequency is equal to complex impedance V  
 $= R + j(X_L - X_C)$

Where

$$X_L = \omega L$$

$$X_C = 1/\omega C$$

### **Resonance Curve:**

The curve between current and frequency is known as resonance curve. The shapes of such curve for of R as shown in fig(1). For smaller values of R, current Vs frequency wave is sharply peak, but for larger values of R, it is flat.

### **Bandwidth of a Resonance Circuit:**

Bandwidth of a circuit is given by the band of frequencies which lies between two points on either side of resonance frequency, where current falls through  $1/\sqrt{2}$  of the maximum value of resonance. Narrow is the bandwidth, higher the selectivity of the circuit. As shown in fig, the bandwidth AB is given by  $F_2 - F_1$ .  $F_1$  is the lower cut off frequency and  $F_2$  is the upper cut off frequency.

### **Q - Factor:**

In the case of a RLC series circuit, it is defined as equal to the voltage magnification in the circuit at resonance. At resonance, current is maximum.  $I_o = V/R$ .

$$\begin{aligned} \text{The applied voltage } V &= I_o R \\ \text{Voltage magnification} &= V_L/V = I_o X_L \end{aligned}$$


In the case of resonance, high Q factor means not only high voltage, but also higher sensitivity of tuning circuit. Q factor can be increased by having a coil of large inductance, not of smaller ohmic resistance.

$$Q = \omega L / R$$


### **Procedure:**

1. Connections are made as per the circuit diagram.
2. By varying the frequency and note down the corresponding meter reading.
3. Draw the current Vs frequency curve and measure the bandwidth, resonance frequency and Q factor.


### **RLC Parallel Resonance Circuit:**

 

**RLC Series Resonance Circuit:**

 


**Series Resonance Curve:**

 

Bandwidth  $B. W = F_2 - F_1$   
 Resonant Frequency =  $F_0$

**Parallel Resonance Curve:**

 

**Tabulation:**

**Series circuit:**

**Input Voltage: V**

**Parallel circuit:**

**Input Voltage: V**

S.No	Frequency (Hertz)	Output Voltage (V)	Current (mA)	S.No	Frequency (Hertz)	Output Voltage (V)	Current (mA)

**PRE REQUISITE**

1. What is a parallel resonant circuit?
2. What is a series resonant circuit?
3. What are tuned circuits?
4. When the circuit is said to be in resonance?
5. What is resonant frequency?

**Review Questions:**

1. Explain series resonance.
2. Define Q factor.
3. What is coefficient of coupling?
4. What is transient response?
5. Briefly explain the series & parallel connection of independent source.

**Result:**

Thus the frequency curve of series and parallel circuits are drawn.

**Ex.No:13**

**TRANSIENT ANALYSIS OF RL & RC CIRCUITS**

**AIM:** To construct and verify the output waveforms of differentiator and integrator circuit

**APPARATUS REQUIRED:**

S.No	COMPONENTS	RANGE	QUANTITY
1	Resistor	10k $\Omega$	1
2	Capacitor	0.01 $\mu$ F	1
3	AFG	(0-1 )MHz	1
4	CRO	(0 – 30 )MHz	1
5	Bread Board		1

**THEORY:**


The RC linear network used for wave shaping circuit based on input frequency is divided as High Pass Filter and Low Pass Filter. The High pass filter acts as differentiator when the time constant is very low. The Low pass filter circuit with a very high time constant acts as an integrator.

**PROCEDURE:**


1. Connect the components and apparatus as shown in the circuit diagram.
2. For *Differentiator* set sinusoidal input of 4 volts and 200Hz and verify the output using CRO. Repeat it with square waveform as an input.
3. For *Integrator* set sinusoidal input of 4 volts and 5 kHz and verify the output using CRO. Repeat it with square waveform as an input. 4. Plot the input and output waveform for differentiator and integrator in linear graph.

**CIRCUIT DIAGRAM**

**INTEGRATOR**

 


**MODEL GRAPH**

 


**CIRCUIT DIAGRAM**

**DIFFERENTIATOR**

 

**MODEL GRAPH**

 

### **PRE REQUISITE**

1. Give the expression for quality factor of series RLC Circuit.
2. Give the expression for quality factor of parallel RLC Circuit.
3. What is the formula to find the power factor in a three phase circuits.
4. What is the formula to find the reactive power in three phase circuits?
5. What is the advantage of using three phase rather than using three single phase circuits?

### **REVIEW QUESTIONS:**

1. How high pass RC circuit is used as a differentiator?
2. How low pass RC circuit is used as an integrator?
3. What should be the input for an integrator circuit to obtain the ramp signal in the output?
4. What will be time constant of an integrator to obtain saw tooth waveform in the output?
5. What is the formula to verify the output of an integrator and a differentiator circuit?

### **RESULT:**

Thus the integrator and the differentiator circuit operation are verified for the square and sine wave input.